

Arithmetic Operations


Signed Integer

- 3 major representations:
 - Sign and magnitude
 - One's complement
 - Two's complement
- Assumptions:
 - 4-bit machine word
 - 16 different values can be represented
 - Roughly half are positive, half are negative

Sign and Magnitude Representation

High order bit is sign: 0 = positive (or zero), 1 = negative
Three low order bits is the magnitude: 0 (000) thru 7 (111)
Number range for n bits = $\pm 2^{n-1} - 1$
Two representations for 0


One's Complement Representation

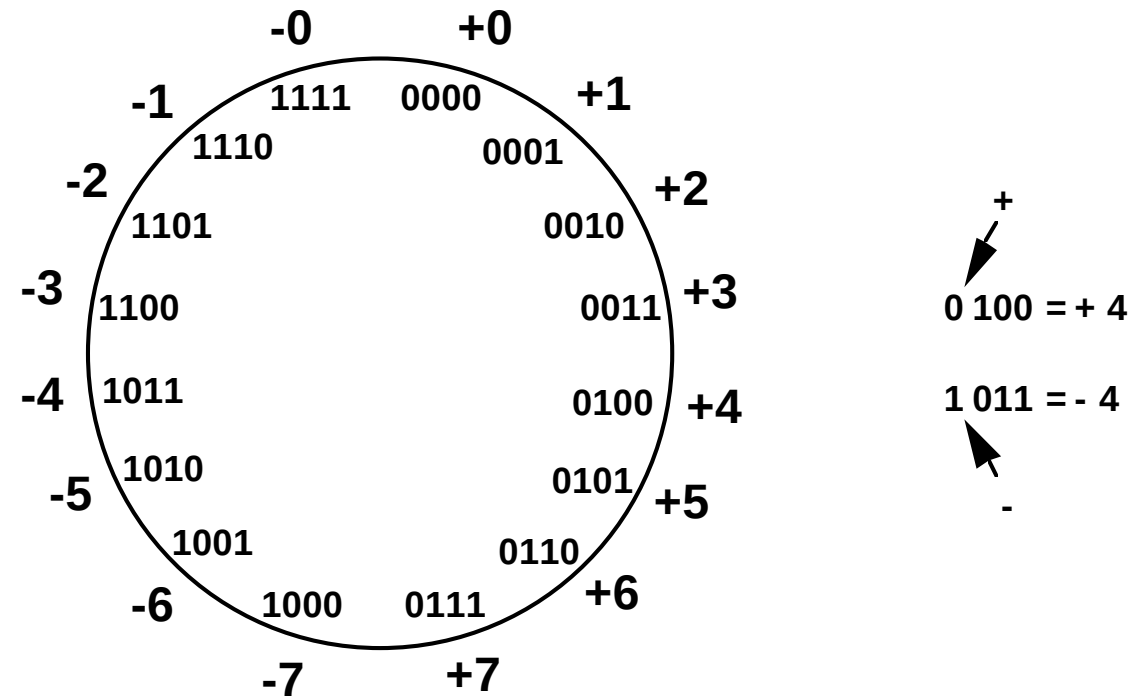

- Subtraction implemented by addition & 1's complement
- Still two representations of 0! This causes some problems
- Some complexities in addition

Two's Complement Representation

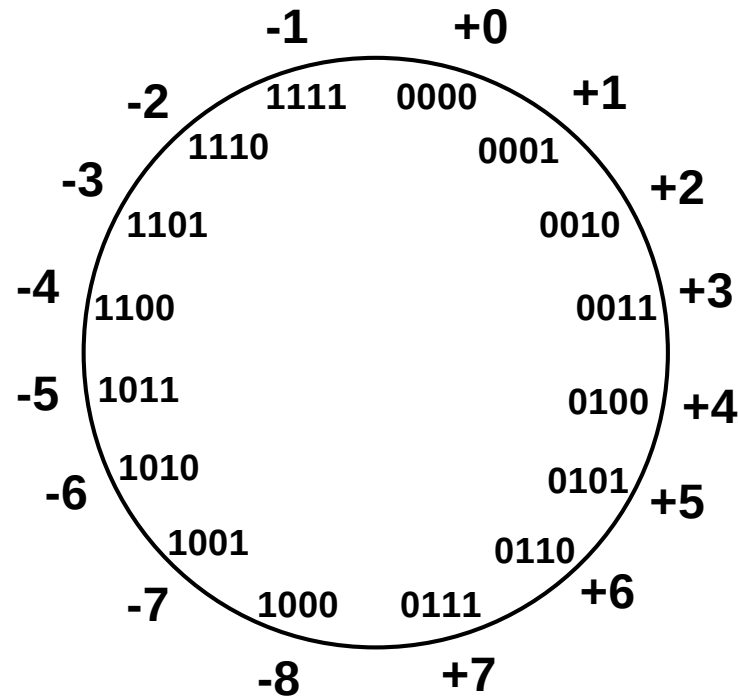*like 1's comp
except shifted
one position
clockwise*



$\begin{matrix} + \\ \swarrow \\ 0\ 100 = +4 \end{matrix}$
 $\begin{matrix} \nwarrow \\ 1\ 100 = -4 \\ - \end{matrix}$

- Only one representation for 0
- One more negative number than positive number

Binary, Signed-Integer Representations

<i>B</i>				Values represented		
b_3	b_2	b_1	b_0	Sign and magnitude	1's complement	2's complement
0	1	1	1	+ 7	+ 7	+ 7
0	1	1	0	+ 6	+ 6	+ 6
0	1	0	1	+ 5	+ 5	+ 5
0	1	0	0	+ 4	+ 4	+ 4
0	0	1	1	+ 3	+ 3	+ 3
0	0	1	0	+ 2	+ 2	+ 2
0	0	0	1	+ 1	+ 1	+ 1
0	0	0	0	+ 0	+ 0	+ 0
1	0	0	0	- 0	- 7	- 8
1	0	0	1	- 1	- 6	- 7
1	0	1	0	- 2	- 5	- 6
1	0	1	1	- 3	- 4	- 5
1	1	0	0	- 4	- 3	- 4
1	1	0	1	- 5	- 2	- 3
1	1	1	0	- 6	- 1	- 2
1	1	1	1	- 7	- 0	- 1

Figure 2.1. Binary, signed-integer representations.

Addition and Subtraction – 2's Complement

If carry-in to the high order bit = carry-out then ignore carry

if carry-in differs from carry-out then overflow

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline \end{array}$$

$$7 \quad 0111$$

$$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline \end{array}$$

$$\begin{array}{r} -7 \quad 11001 \\ \hline \end{array}$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline \end{array}$$

$$1 \quad 10001$$

$$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline \end{array}$$

$$\begin{array}{r} -1 \quad 1111 \end{array}$$



Simpler addition scheme makes two's complement the most common choice for integer number systems within digital systems

2's-Complement Add and Subtract Operations

(a)	$\begin{array}{r} 0010 \\ + 0011 \\ \hline \end{array}$	$\begin{array}{r} (+2) \\ (+3) \\ \hline \end{array}$		(b)	$\begin{array}{r} 0100 \\ + 1010 \\ \hline \end{array}$	$\begin{array}{r} (+4) \\ (-6) \\ \hline \end{array}$
	$\begin{array}{r} 0101 \\ \hline \end{array}$	$\begin{array}{r} (+5) \\ \hline \end{array}$			$\begin{array}{r} 1110 \\ \hline \end{array}$	$\begin{array}{r} (-2) \\ \hline \end{array}$
(c)	$\begin{array}{r} 1011 \\ + 1110 \\ \hline \end{array}$	$\begin{array}{r} (-5) \\ (-2) \\ \hline \end{array}$		(d)	$\begin{array}{r} 0111 \\ + 1101 \\ \hline \end{array}$	$\begin{array}{r} (+7) \\ (-3) \\ \hline \end{array}$
	$\begin{array}{r} 1001 \\ \hline \end{array}$	$\begin{array}{r} (-7) \\ \hline \end{array}$			$\begin{array}{r} 0100 \\ \hline \end{array}$	$\begin{array}{r} (+4) \\ \hline \end{array}$
(e)	$\begin{array}{r} 1101 \\ - 1001 \\ \hline \end{array}$	$\begin{array}{r} (-3) \\ (-7) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 1101 \\ + 0111 \\ \hline \end{array}$	
					$\begin{array}{r} 0100 \\ \hline \end{array}$	$\begin{array}{r} (+4) \\ \hline \end{array}$
(f)	$\begin{array}{r} 0010 \\ - 0100 \\ \hline \end{array}$	$\begin{array}{r} (+2) \\ (+4) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 0010 \\ + 1100 \\ \hline \end{array}$	
					$\begin{array}{r} 1110 \\ \hline \end{array}$	$\begin{array}{r} (-2) \\ \hline \end{array}$
(g)	$\begin{array}{r} 0110 \\ - 0011 \\ \hline \end{array}$	$\begin{array}{r} (+6) \\ (+3) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 0110 \\ + 1101 \\ \hline \end{array}$	
					$\begin{array}{r} 0011 \\ \hline \end{array}$	$\begin{array}{r} (+3) \\ \hline \end{array}$
(h)	$\begin{array}{r} 1001 \\ - 1011 \\ \hline \end{array}$	$\begin{array}{r} (-7) \\ (-5) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 1001 \\ + 0101 \\ \hline \end{array}$	
					$\begin{array}{r} 1110 \\ \hline \end{array}$	$\begin{array}{r} (-2) \\ \hline \end{array}$
(i)	$\begin{array}{r} 1001 \\ - 0001 \\ \hline \end{array}$	$\begin{array}{r} (-7) \\ (+1) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 1001 \\ + 1111 \\ \hline \end{array}$	
					$\begin{array}{r} 1000 \\ \hline \end{array}$	$\begin{array}{r} (-8) \\ \hline \end{array}$
(j)	$\begin{array}{r} 0010 \\ - 1101 \\ \hline \end{array}$	$\begin{array}{r} (+2) \\ (-3) \\ \hline \end{array}$	$\Rightarrow$		$\begin{array}{r} 0010 \\ + 0011 \\ \hline \end{array}$	
					$\begin{array}{r} 0101 \\ \hline \end{array}$	$\begin{array}{r} (+5) \\ \hline \end{array}$

Figure 2.4. 2's-complement Add and Subtract operations.

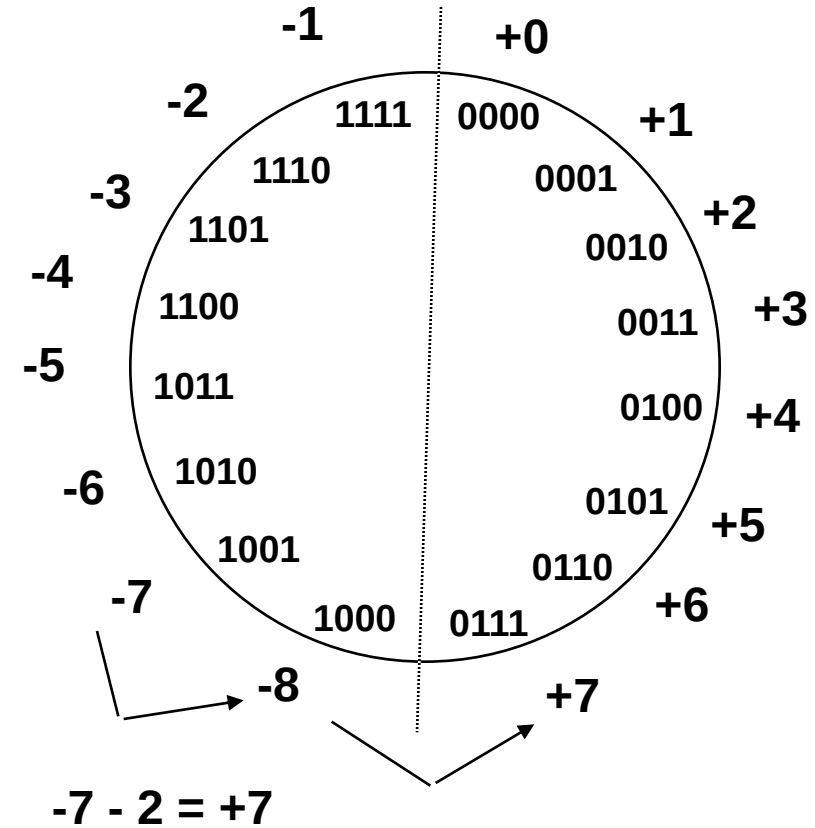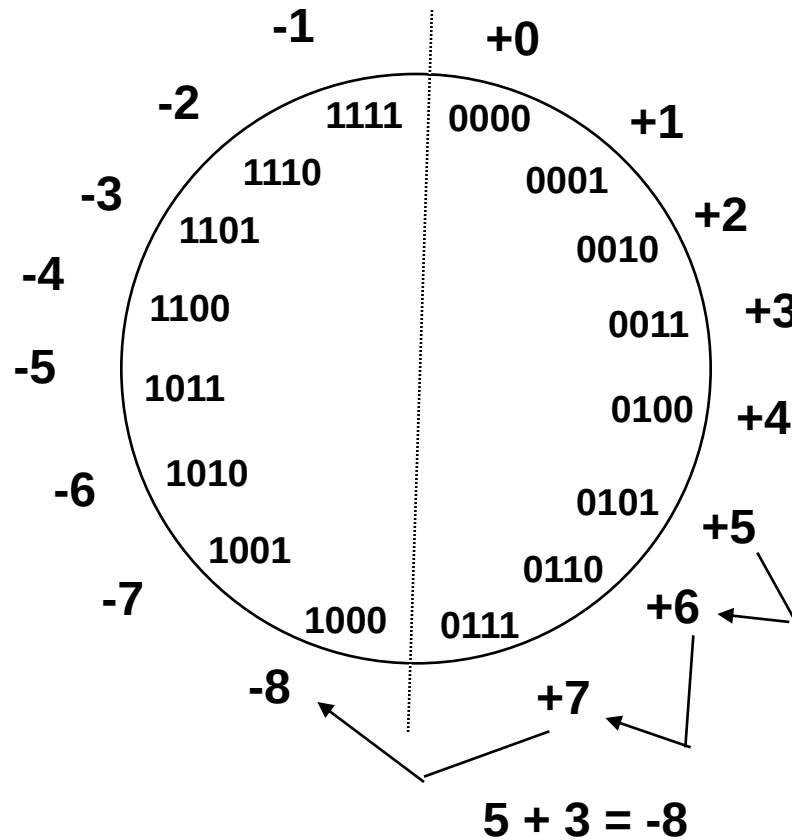Overflow - Add two positive numbers to get a negative number or two negative numbers to get a positive number



Overflow Conditions

$$\begin{array}{r}
 5 \qquad 0111 \\
 \quad \quad 0101 \\
 \hline
 \underline{3} \qquad \underline{0011} \\
 -8 \qquad 1000
 \end{array}$$

Overflow

$$\begin{array}{r}
 5 \qquad 0000 \\
 \quad \quad 0101 \\
 \hline
 \underline{2} \qquad \underline{0010} \\
 7 \qquad 0111
 \end{array}$$

No overflow

$$\begin{array}{r}
 -7 \qquad 1000 \\
 \quad \quad 1001 \\
 \hline
 \underline{-2} \qquad \underline{1100} \\
 7 \qquad 10111
 \end{array}$$

Overflow

$$\begin{array}{r}
 -3 \qquad 1111 \\
 \quad \quad 1101 \\
 \hline
 \underline{-5} \qquad \underline{1011} \\
 -8 \qquad 11000
 \end{array}$$

No overflow

- Overflows can occur when the sign of the two operands is the same.
- Overflow occurs if the sign of the result is different from the sign of the operands.
- Overflow when carry-in to the high-order bit does not equal carry out

Addition and Subtraction of Signed Numbers

Addition/subtraction of signed Numbers

x_i	y_i	Carry-in c_i	Sum s_i	Carry-out c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

At the i^{th} stage:

Input:

c_i is the carry-in

Output:


s_i is the sum

c_{i+1} carry-out to $(i+1)^{st}$ state


$$s_i = \overline{x_i} \overline{y_i} c_i + \overline{x_i} y_i \overline{c_i} + x_i \overline{y_i} \overline{c_i} + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

Example:

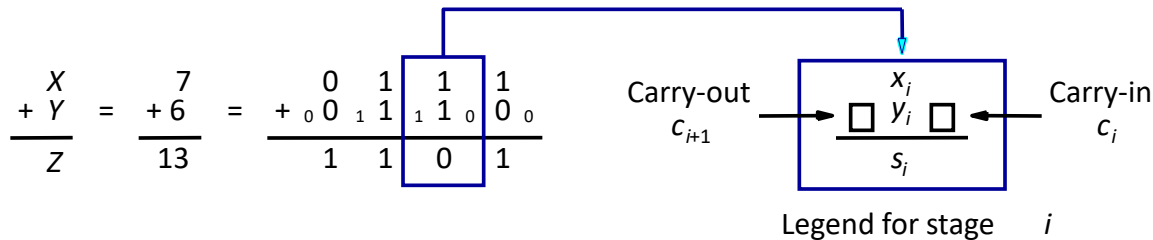


Addition logic for a single stage

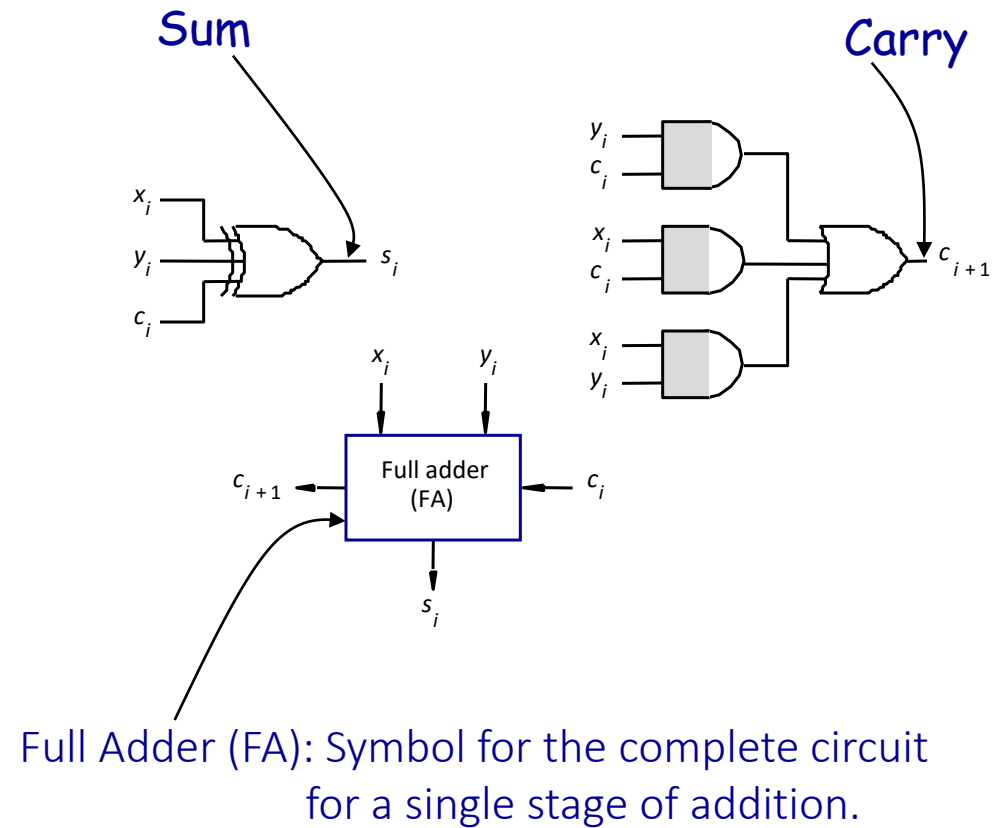

n -bit adder

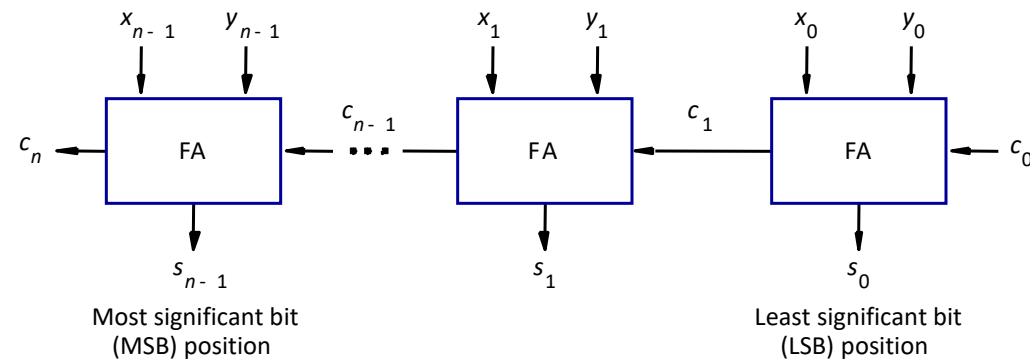
- Cascade n full adder (FA) blocks to form a n -bit adder.
- Carries propagate or ripple through this cascade, [n-bit ripple carry adder](#).



Carry-in c_0 into the LSB position provides a convenient way to perform subtraction.

K n -bit adder

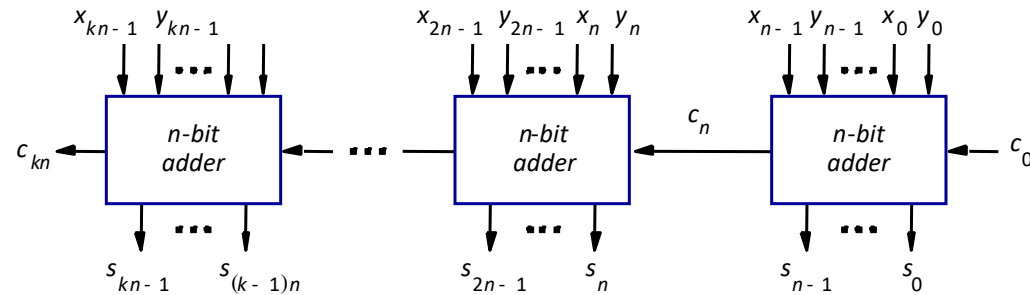K n -bit numbers can be added by cascading k n -bit adders.




Each n -bit adder forms a block, so this is cascading of blocks.


Carries ripple or propagate through blocks, [Blocked Ripple Carry Adder](#)

n -bit subtractor

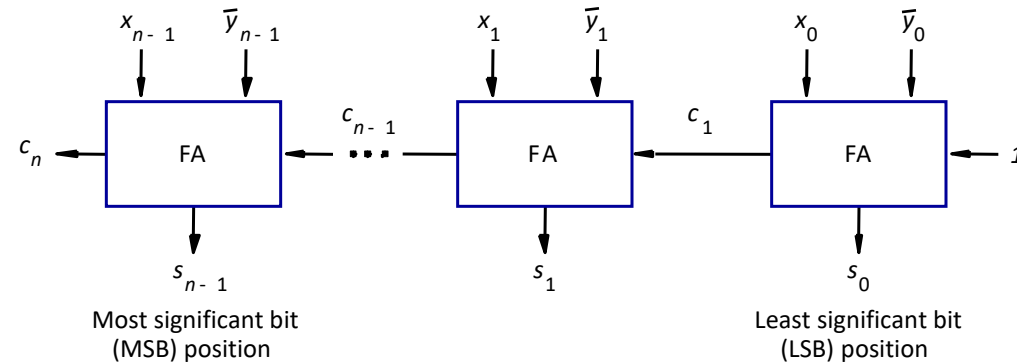- Recall $X - Y$ is equivalent to adding 2's complement of Y to X .
- 2's complement is equivalent to 1's complement + 1.
- $X - Y = X + \bar{Y} + 1$
- 2's complement of positive and negative numbers is computed similarly.



n -bit adder/subtractor (contd..)

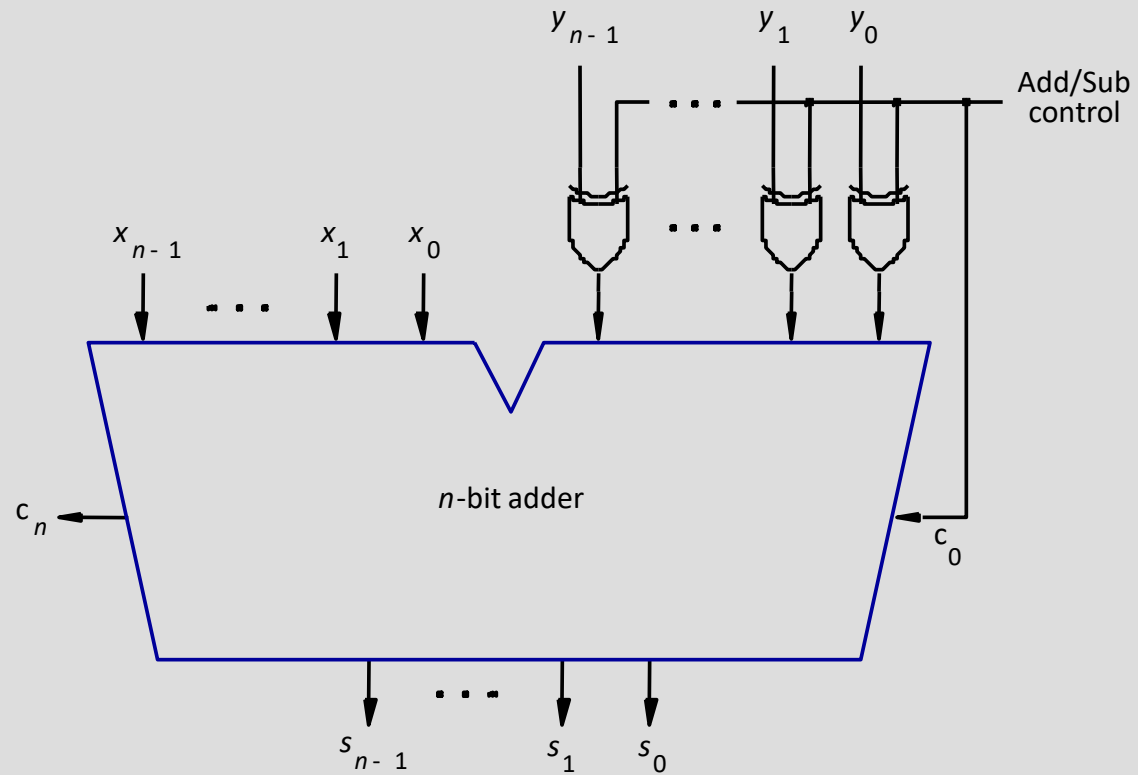

- Add/sub control = 0, addition.
- Add/sub control = 1, subtraction.


Detecting overflows

- Overflows can only occur when the sign of the two operands is the same.
- Overflow occurs if the sign of the result is different from the sign of the operands.
- Recall that the MSB represents the sign.
 - $x_{n-1}, y_{n-1}, s_{n-1}$ represent the sign of operand x , operand y and result sum s respectively.
- Circuit to detect overflow can be implemented by the following logic expressions:

$$\text{Overflow} = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$


$$\text{Overflow} = c_n \oplus c_{n-1}$$

Computing the add time

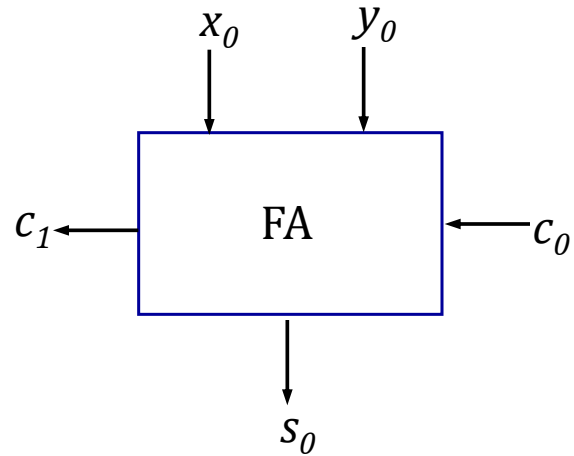


Consider 0^{th} stage:

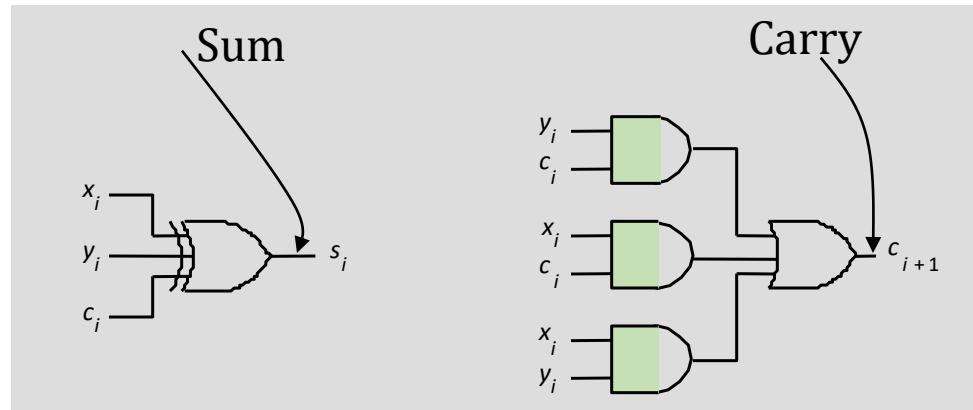- c_1 is available after 2 gate delays.
- s_1 is available after 1 gate delay.



Computing the add time (contd..)

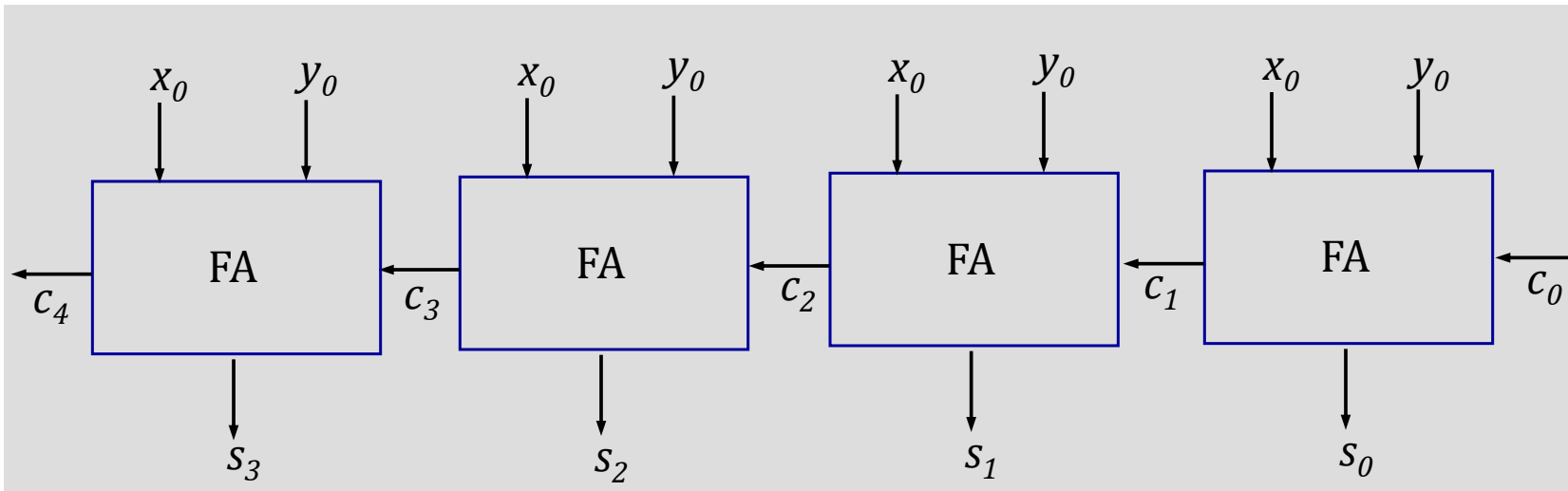Cascade of 4 Full Adders, or a 4-bit adder



- s_0 available after 1 gate delays, c_1 available after 2 gate delays.
- s_1 available after 3 gate delays, c_2 available after 4 gate delays.
- s_2 available after 5 gate delays, c_3 available after 6 gate delays.
- s_3 available after 7 gate delays, c_4 available after 8 gate delays.

For an n -bit adder, s_{n-1} is available after $2n-1$ gate delays
 c_n is available after $2n$ gate delays.

Fast addition

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$
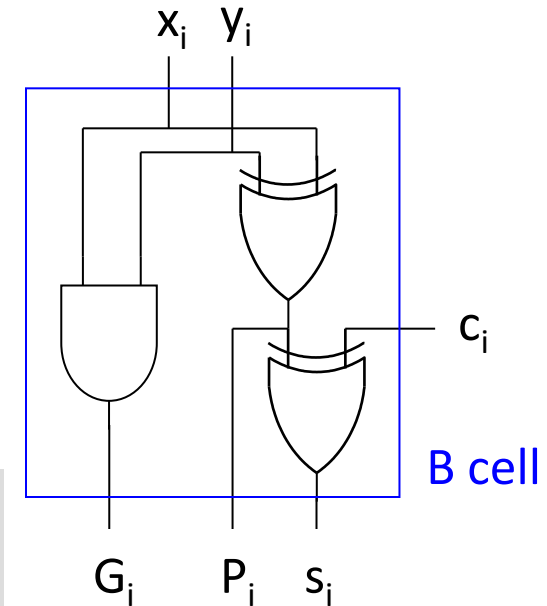
$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$



- G_i is called generate function and P_i is called propagate function
- G_i and P_i are computed only from x_i and y_i and not c_i , thus they can be computed in one gate delay after X and Y are applied to the inputs of an n -bit adder.
- $c_{i+1} = 1$ only when Generate = 1 and Propagate = 0 or 1
- So we can modify the P_i

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i \oplus y_i$$

Carry lookahead

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing


$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$

until


$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- All carries can be obtained 3 gate delays after X , Y and c_0 are applied.
 - One gate delay for P_i and G_i
 - Two gate delays in the AND-OR circuit for c_{i+1}
- All sums can be obtained 1 gate delay after the carries are computed.
- Independent of n , n -bit addition requires only 4 gate delays.
- This is called Carry Lookahead adder.

Carry-lookahead adder

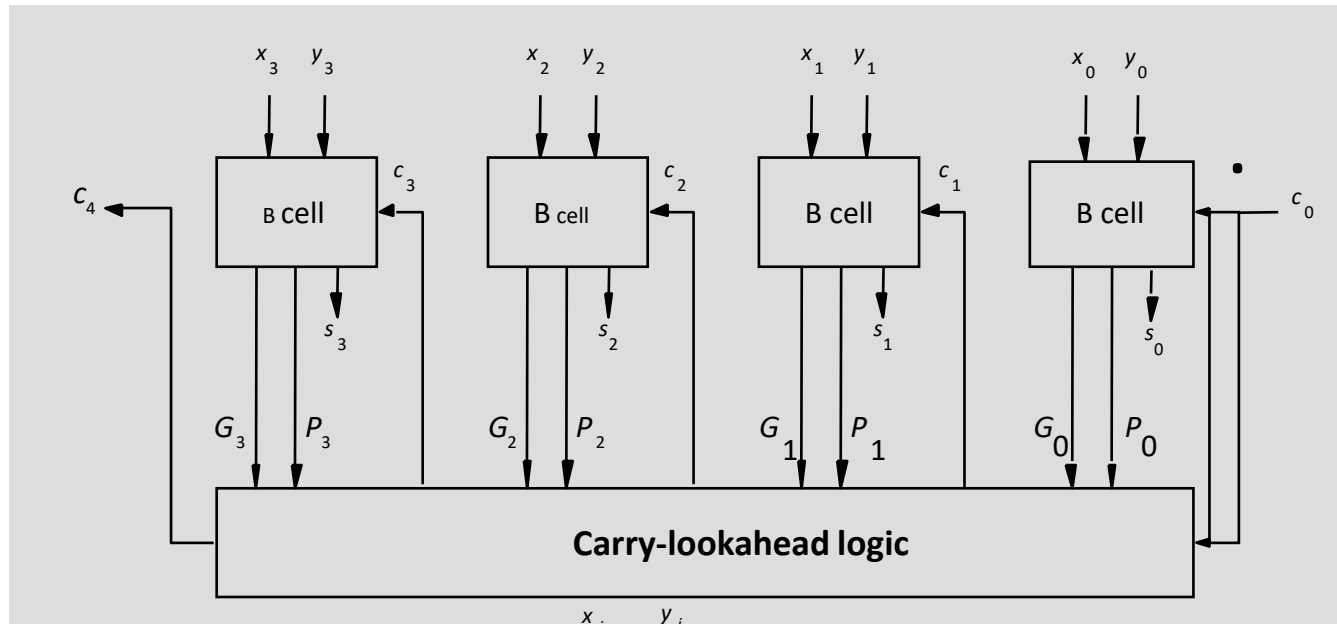

**4-bit
carry-lookahead
adder**

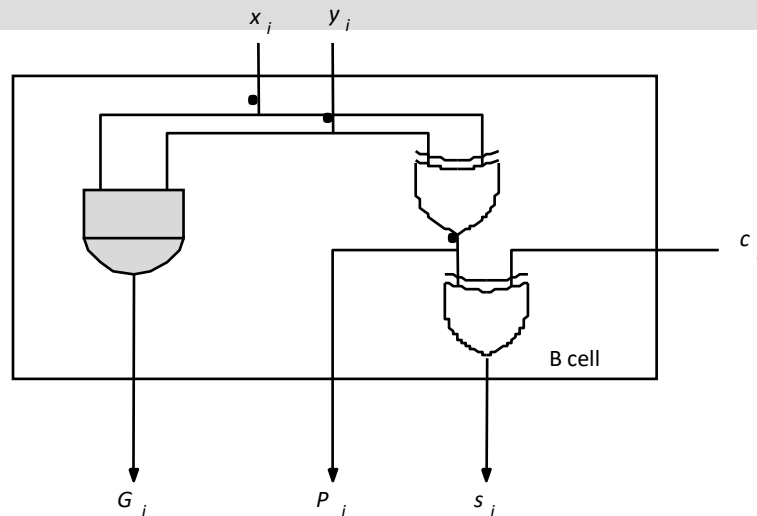

B-cell for a single stage


Carry lookahead adder (contd..)

- Performing n -bit addition in 4 gate delays independent of n is good only theoretically because of fan-in constraints.

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- Last AND gate and OR gate require a fan-in of $(n+1)$ for a n -bit adder.
 - For a 4-bit adder ($n=4$) fan-in of 5 is required.
 - Practical limit for most gates.
- In order to add operands longer than 4 bits, we can cascade 4-bit Carry-Lookahead adders. Cascade of Carry-Lookahead adders is called Blocked Carry-Lookahead adder.
- Fan-in is the number of inputs a gate can handle.

4-bit carry-lookahead Adder

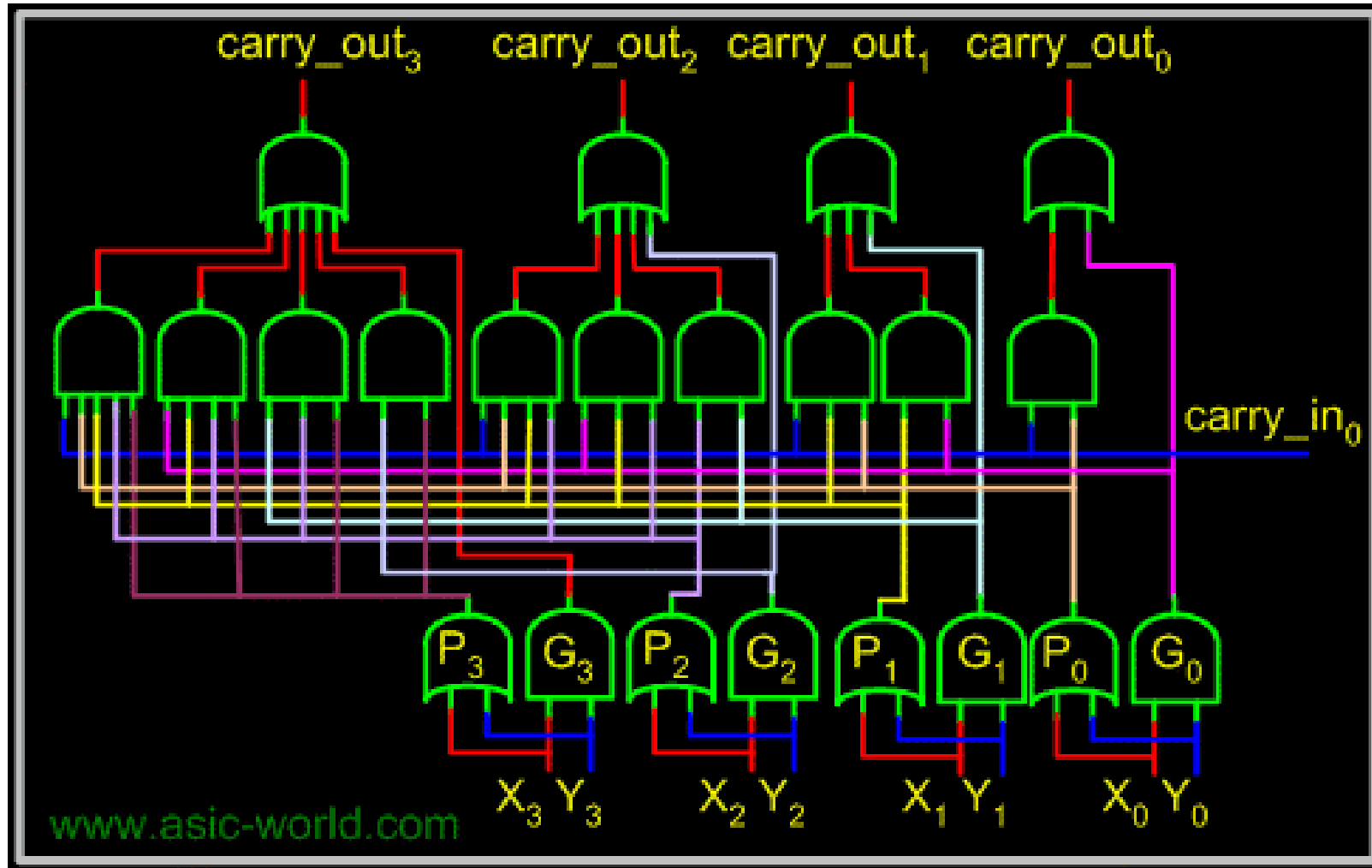

Blocked Carry-Lookahead adder

Carry-out from a 4-bit block can be given as:

$$c_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

Rewrite this as:

$$P_0^I = P_3P_2P_1P_0$$


$$G_0^I = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$$

Subscript I denotes the blocked carry lookahead and identifies the block.

Cascade 4 4-bit adders, c_{16} can be expressed as:

$$c_{16} = G_3^I + P_3^I G_2^I + P_3^I P_2^I G_1^I + P_3^I P_2^I P_1^0 G_0^I + P_3^I P_2^I P_1^0 P_0^0 c_0$$

Blocked Carry-Lookahead adder

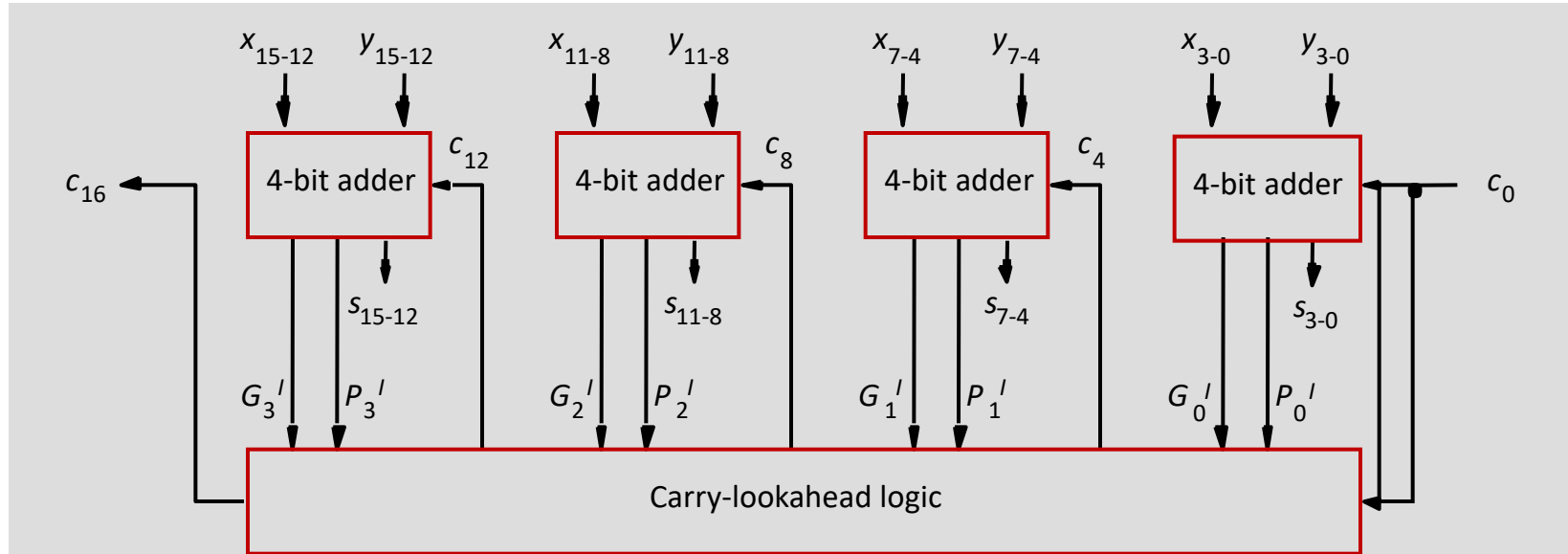

After x_i , y_i and c_0 are applied as inputs:

- G_i and P_i for each stage are available after 1 gate delay.
- P^I is available after 2 and G^I after 3 gate delays.
- All carries are available after 5 gate delays.
- c_{16} is available after 5 gate delays.
- s_{15} which depends on c_{12} is available after 8 (5+3) gate delays
(Recall that for a 4-bit carry lookahead adder, the last sum bit is available 3 gate delays after all inputs are available)

Multiplication

Multiplication of unsigned numbers

1	1	0	1	(13) Multiplicand M
1	0	1	1	(11) Multiplier Q
1	1	0	1	
1	1	0	1	
0	0	0	0	
1	1	0	1	
1	0	0	0	1
1	0	0	0	1
1	0	0	0	1
1	0	0	0	1

Product of 2 n -bit numbers is at most a $2n$ -bit number.


Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.

Multiplication of unsigned numbers (contd..)

- We added the partial products at end.
 - Alternative would be to add the partial products at each stage.
- Rules to implement multiplication are:
 - If the i^{th} bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
 - Hand over the partial product to the next stage
 - Value of the partial product at the start stage is 0.

Multiplication of unsigned numbers

Typical multiplication cell


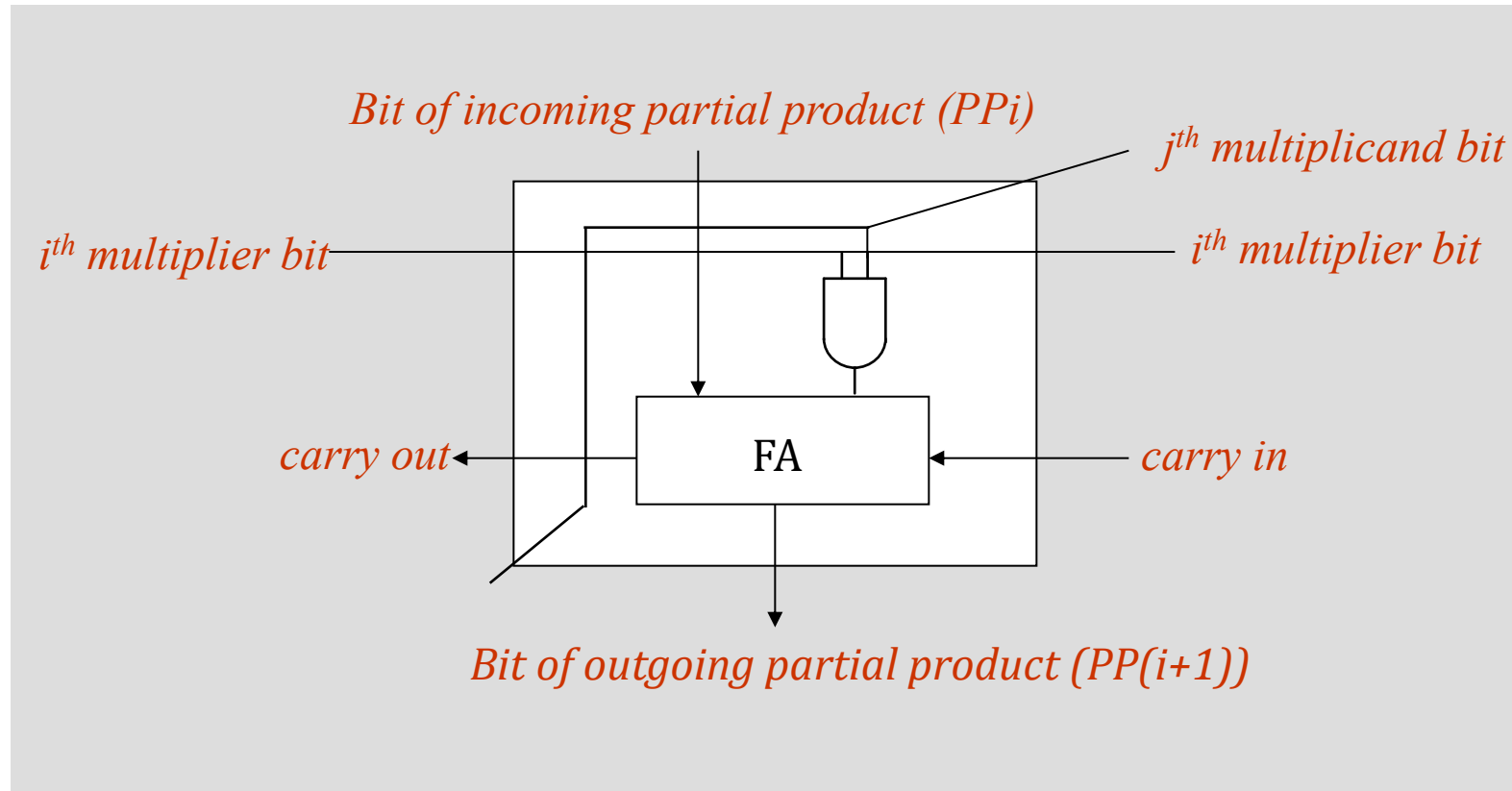


Typical multiplication cell

- The main component in each cell is a full adder, FA.
- The AND gate in each cell determines whether a multiplicand bit, m_j , is added to the incoming partial-product bit, based on the value of the multiplier bit, q_i .
- Each row i , where $0 \leq i \leq 3$, adds the multiplicand (appropriately shifted) to the incoming partial product, PP_i , to generate the outgoing partial product, $PP(i + 1)$, if $q_i = 1$.
- If $q_i = 0$, PP_i is passed vertically downward unchanged.
- PP_0 is all 0s, and PP_4 is the desired product.
- The multiplicand is shifted left one position per row by the diagonal signal path.

Combinatorial array multiplier

Combinatorial array multiplier

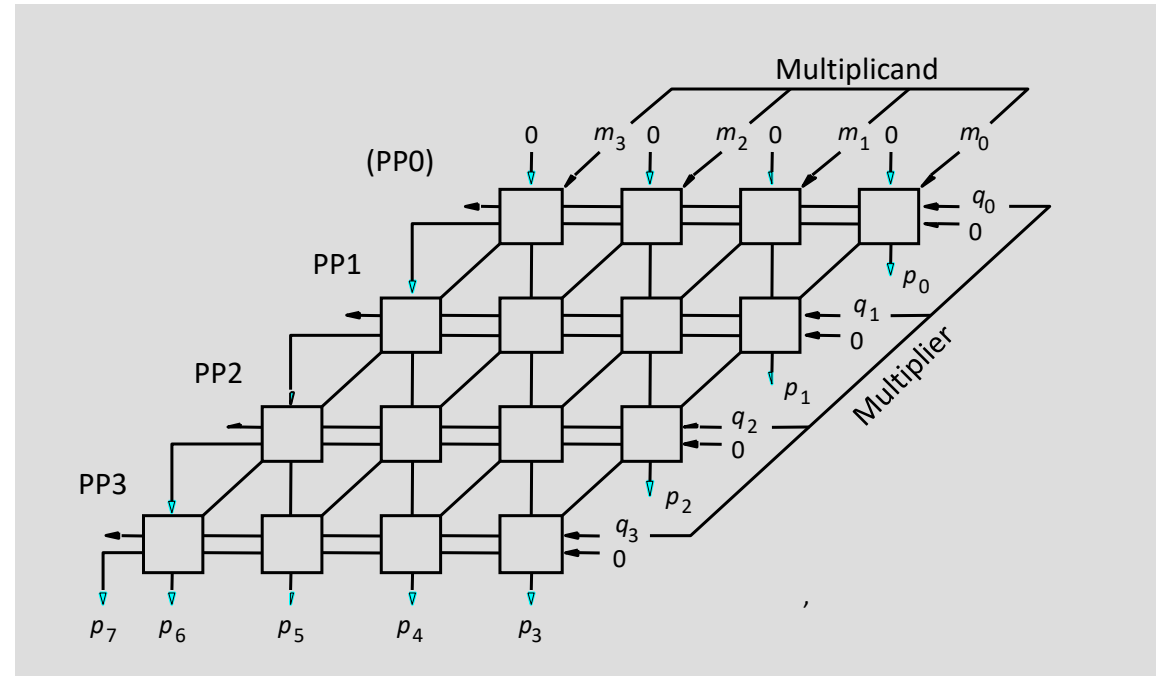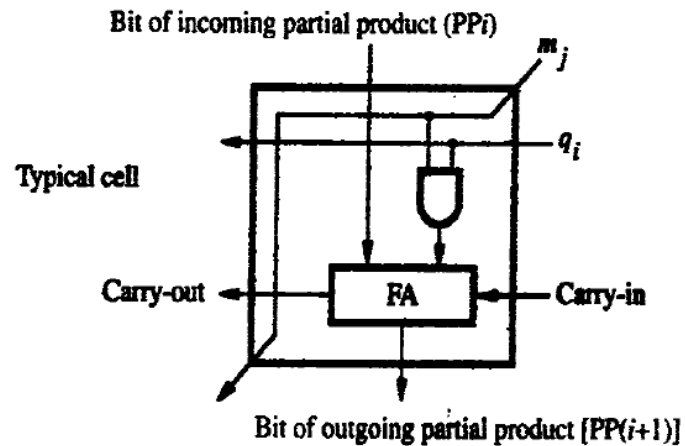

Product is: $p_7 p_6 \dots p_0$

Multiplicand is shifted by displacing it through an array of adders.


Combinatorial array multiplier (contd..)

- Combinatorial array multipliers are:
 - Extremely inefficient.
 - Have a high gate count for multiplying numbers of practical size such as 32-bit or 64-bit numbers.
 - Perform only one function, namely, unsigned integer product.
- Improve gate efficiency by using a mixture of combinatorial array techniques and sequential techniques requiring less combinational logic.

Sequential multiplication

- Recall the rule for generating partial products:
 - If the i th bit of the multiplier is 1, add the appropriately shifted multiplicand to the current partial product.
 - Multiplicand has been shifted left when added to the partial product.
- However, adding a left-shifted multiplicand to an unshifted partial product is equivalent to adding an unshifted multiplicand to a right-shifted partial product.


Sequential Circuit Multiplier

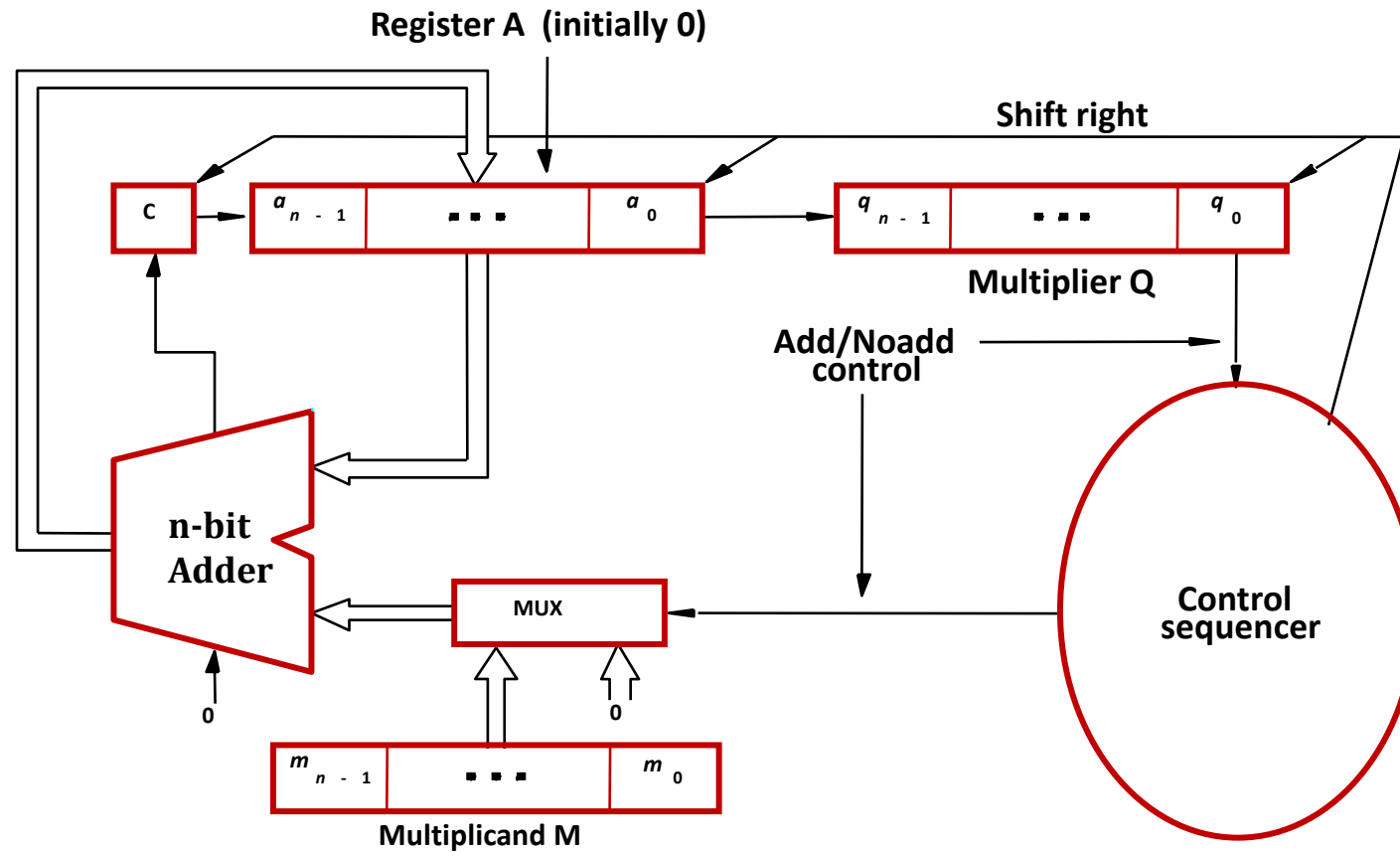

Sequential Circuit Multiplier

- Registers A and Q are shift registers, concatenated as shown. Together, they hold partial product PP_i while multiplier bit q_i generates the signal Add/No add.
- This signal causes the multiplexer MUX to select 0 when $q_i = 0$, or to select the multiplicand M when $q_i = 1$, to be added to PP_i to generate $PP(i + 1)$.
- The product is computed in n cycles. The partial product grows in length by one bit per cycle from the initial vector, PP_0 , of n 0s in register A.
- The carry-out from the adder is stored in flip-flop C, shown at the left end of register A.
- At the start, the multiplier is loaded into register Q, the multiplicand into register M, and C and A are cleared to 0. At the end of each cycle, C, A, and Q are shifted right one bit position to allow for growth of the partial product as the multiplier is shifted out of register Q.
- Because of this shifting, multiplier bit q_i appears at the LSB position of Q to generate the Add/No add signal at the correct time, starting with q_0 during the first cycle, q_1 during the second cycle, and so on.
- After they are used, the multiplier bits are discarded by the right-shift operation. Note that the carry-out from the adder is the leftmost bit of $PP(i + 1)$, and it must be held in the C flip-flop to be shifted right with the contents of A and Q.
- After n cycles, the high-order half of the product is held in register A and the low-order half is in register Q.

Sequential multiplication (contd..)

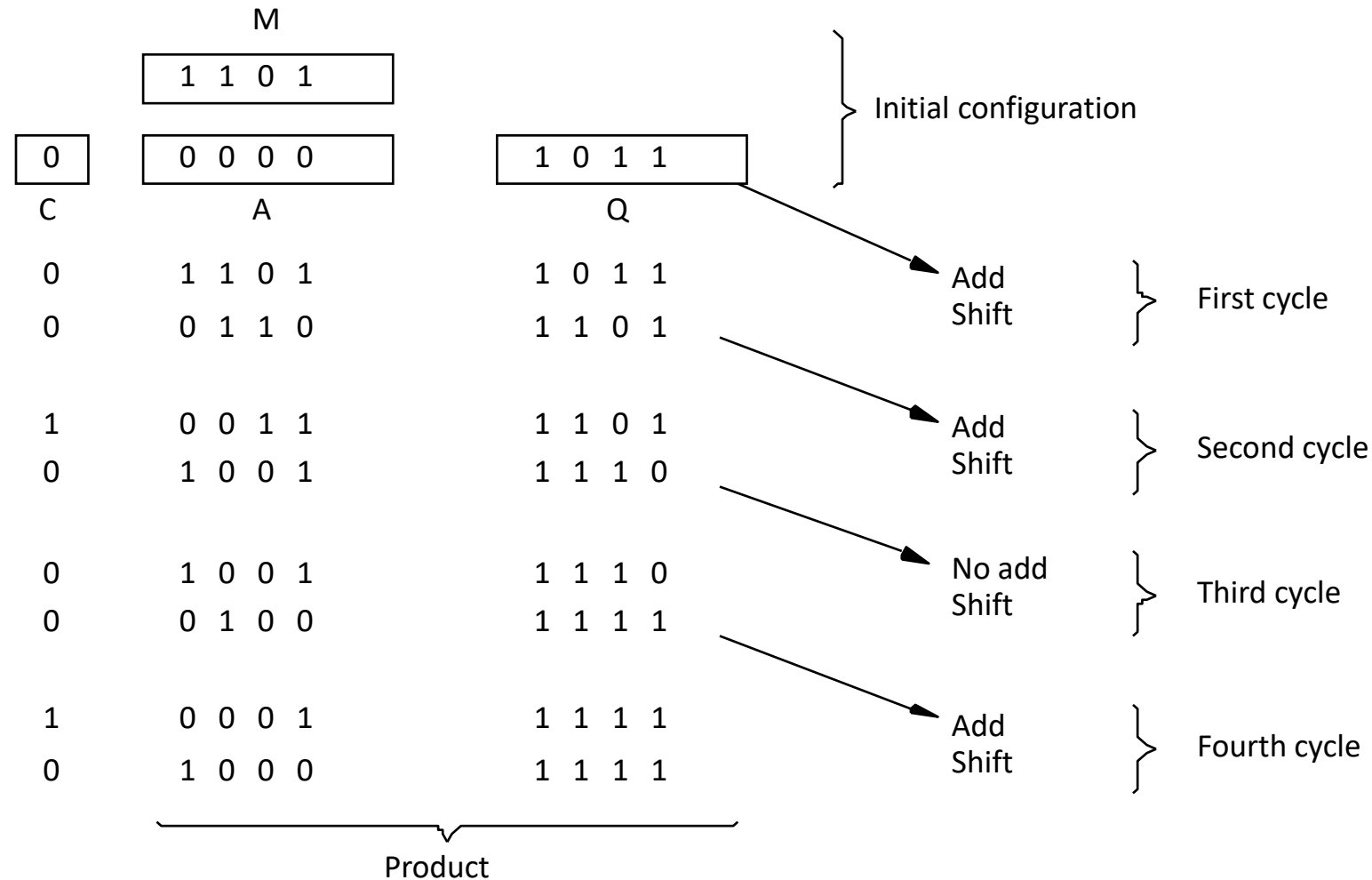

Signed Multiplication

Signed Multiplication

- Considering 2's-complement signed operands, what will happen to $(-13) \times (+11)$ if following the same method of unsigned multiplication?

						1	0	0	1	1	(- 13)
						0	1	0	1	1	(+ 11)
	1	1	1	1	1	1	0	0	1	1	
	1	1	1	1	1	0	0	1	1		
	0	0	0	0	0	0	0	0			
	1	1	1	0	0	1	1				
	0	0	0	0	0	0					
	1	1	0	1	1	1	0	0	0	1	(- 143)

Sign extension is shown in red

Sign extension of negative multiplicand.

Signed Multiplication

- For a negative multiplier, a straightforward solution is to form the 2's-complement of both the multiplier and the multiplicand and proceed as in the case of a positive multiplier.
- This is possible because complementation of both operands does not change the value or the sign of the product.
- A technique that works equally well for both negative and positive multipliers – Booth algorithm.

Booth Algorithm

- In general, in the Booth scheme, -1 times the shifted multiplicand is selected when moving from 0 to 1, and +1 times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	0	
																		
0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	0	

Treats both positive and negative 2's-complement operands uniformly

Algorithm (scanning multiplier right to left)

0 to 1 => add -1 times shifted multiplicand

1 to 0 => add +1 times shifted multiplicand

0 to 0 or 1 to 1 => add 0

Booth Algorithm

$$\begin{array}{r} -4 \quad 1100 \\ \times 5 \quad 0101 \\ \hline -20 \end{array}$$

$$\begin{array}{r} 1 \ 1 \ 0 \ 0 \\ \times 0 \ 1 \ 0 \ 1 \\ \hline +1 -1 +1 -1 \end{array}$$

$$0 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0$$

2's complement of 1100 with signed extension 11111100

$$1 \ 1 \ 1 \ 1 \ 1 \ 0 \ 0$$

Multiplicand 1100 with signed extension 11111100

$$0 \ 0 \ 0 \ 1 \ 0 \ 0$$

2's complement of 1100

$$+ \ 1 \ 1 \ 1 \ 0 \ 0$$

Multiplicand 1100

$$1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0$$

$$0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0 = -20$$

Booth Algorithm

$$\begin{array}{r} 5 \\ \times -4 \\ \hline -20 \end{array}$$

0101
1100

$$\begin{array}{r} 0101 \\ \times 1100 \\ \hline 0-100 \end{array}$$

0 0 0 0 0 0 0 0

0 0 0 0 0 0 0 0

1 1 1 0 1 1

2's complement of 0101

+ 0 0 0 0 0 0

1 1 1 0 1 1 0 0

0 0 0 1 0 1 0 0 = -20

Booth Algorithm

- Consider in a multiplication, the multiplier is positive 0011110, how many appropriately shifted versions of the multiplicand are added in a standard procedure?

							0	1	0	1	1	0	1
							0	0	+1	+1	+1	+1	0
							0	0	0	0	0	0	0
					0		1	0	1	1	0	1	
				0	1		0	1	1	0	1		
			0	1	0		1	1	0	1			
		0	1	0	1		1	0	1				
	0	0	0	0	0		0	0					
0	0	0	0	0	0		0						
0	0	0	1	0	1	0	1	0	0	0	1	1	0

Booth Algorithm

- Since $0011110 = 0100000 - 0000010$, if we use the expression to the right, what will happen?

								0	1	0	1	1	0	1		
								0	+	1	0	0	0	-	1	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	0	1	0	0	1	1			
0	0	0	0	0	0	0	0	0	0	0	0	0	0			
0	0	0	0	0	0	0	0	0	0	0	0	0				
0	0	0	0	0	0	0	0	0	0	0	0					
0	0	0	0	0	0	0	0	0	0	0						
0	0	0	1	0	1	1	0	1								
0	0	0	0	0	0	0	0									
0	0	0	1	0	1	0	1	0	0	0	1	1	0			

2's complement of the multiplicand

Booth Algorithm

$$\begin{array}{r}
 \begin{array}{rcccl}
 & 0 & 1 & 1 & 0 & 1 & (+13) \\
 \times & 1 & 1 & 0 & 1 & 0 & (-6) \\
 \hline
 \end{array}
 & \xrightarrow{\text{Booth}} &
 \begin{array}{rcccl}
 & 0 & 1 & 1 & 0 & 1 \\
 & 0 & -1 & +1 & -1 & 0 \\
 \hline
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\
 1 \ 1 \ 1 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \\
 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\
 1 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \\
 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \quad (-78)
 \end{array}$$

Booth multiplication with a negative multiplier.

Booth Algorithm

Multiplier		Version of multiplicand selected by bit i
Bit i	Bit $i-1$	
0	0	0 $\times M$
0	1	+ 1 $\times M$
1	0	- 1 $\times M$
1	1	0 $\times M$

Booth multiplier recoding table.

Booth Algorithm

- Best case – a long string of 1's (skipping over 1s)
- Worst case – 0's and 1's are alternating

Worst-case multiplier

0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1



Ordinary multiplier

1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0



Good multiplier


0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1
0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1



Fast Multiplication

Bit-Pair Recoding of Multipliers

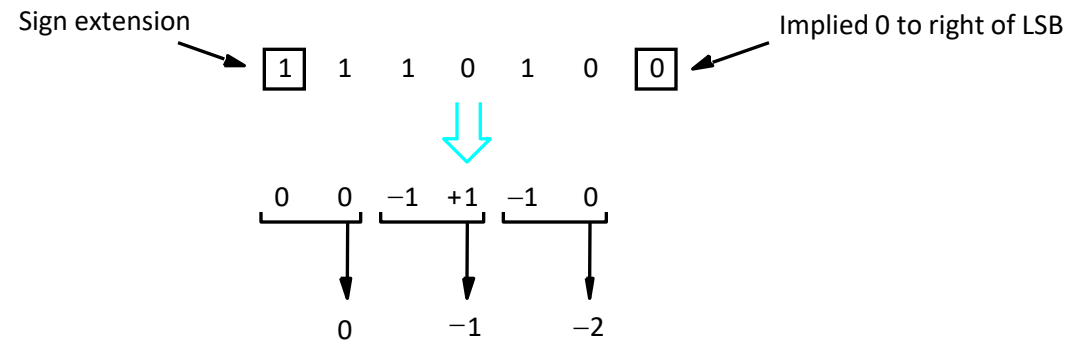- Bit-pair recoding halves the maximum number of summands (versions of the multiplicand).



(a) Example of bit-pair recoding derived from Booth recoding

Bit-Pair Recoding of Multipliers

Multiplier bit-pair		Multiplier bit on the right $i - 1$	Multiplicand selected at position i
$i + 1$	i		
0	0	0	0 X M
0	0	1	+ 1 X M
0	1	0	+ 1 X M
0	1	1	+ 2 X M
1	0	0	- 2 X M
1	0	1	- 1 X M
1	1	0	- 1 X M
1	1	1	0 X M

(b) Table of multiplicand selection decisions

Bit-Pair Recoding of Multipliers


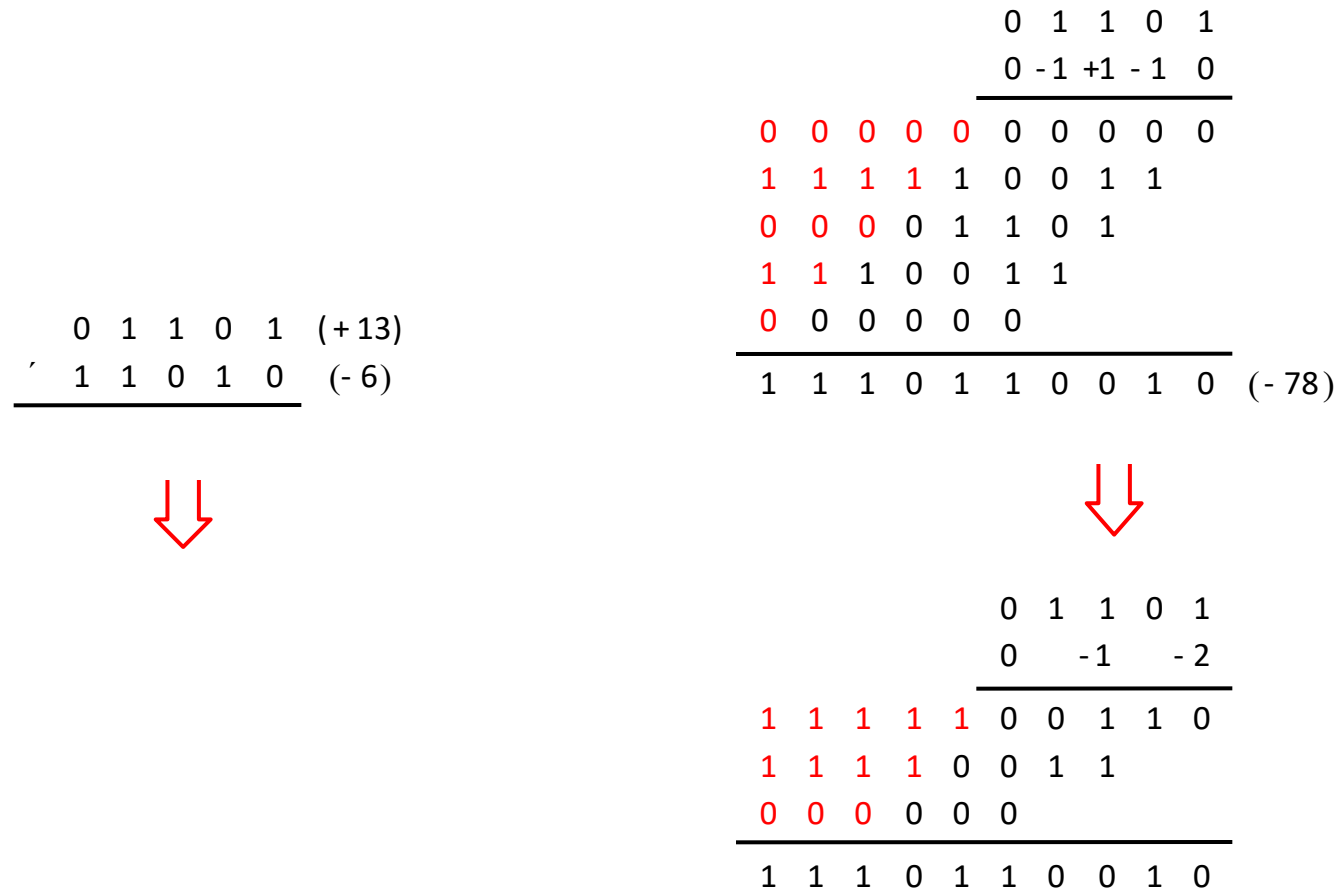



Figure 6.15. Multiplication requiring only $n/2$ summands.

Carry-Save Addition of Summands

- CSA speeds up the addition process.

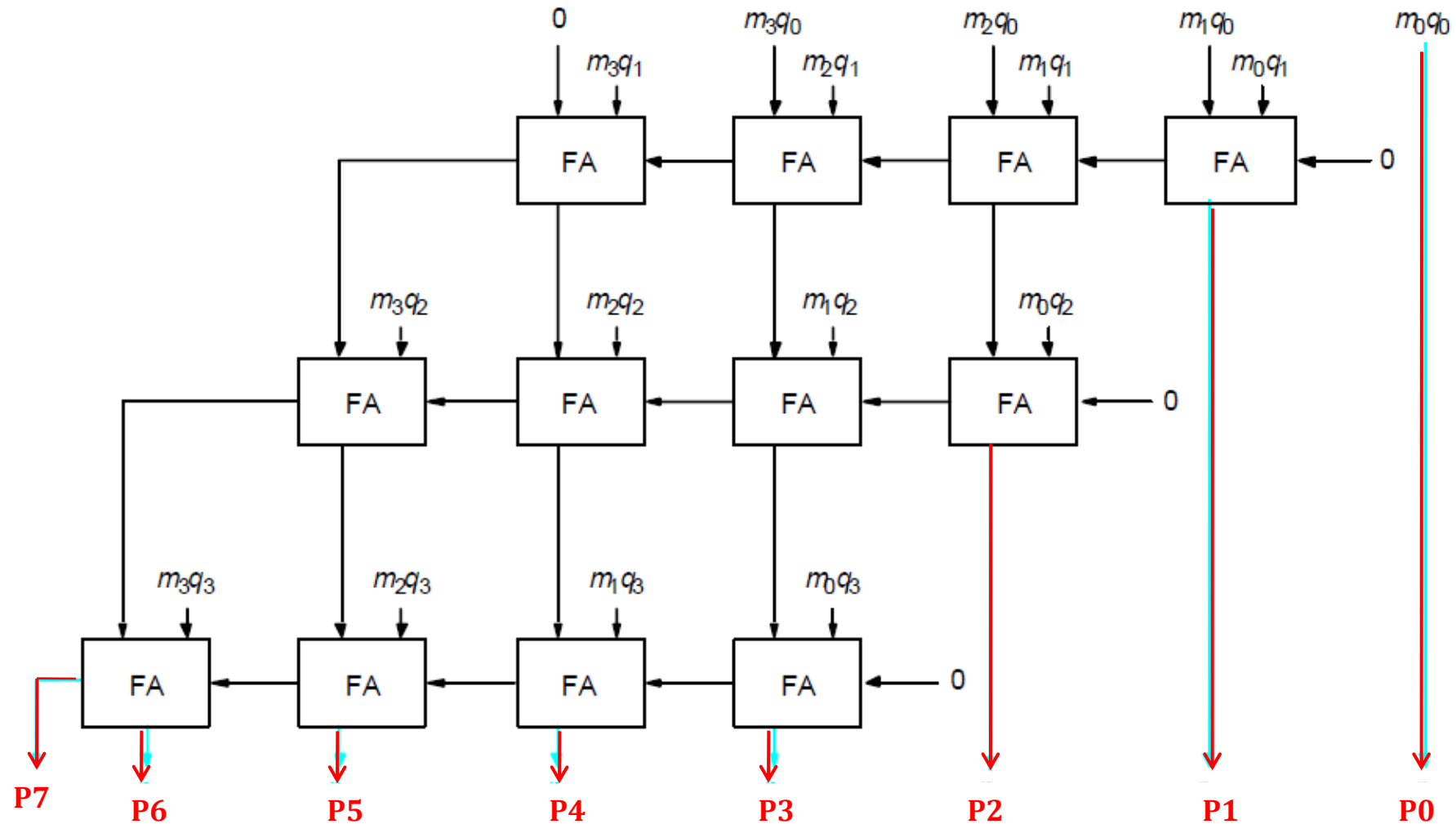

Carry-Save Addition of Summands (Cont.,)

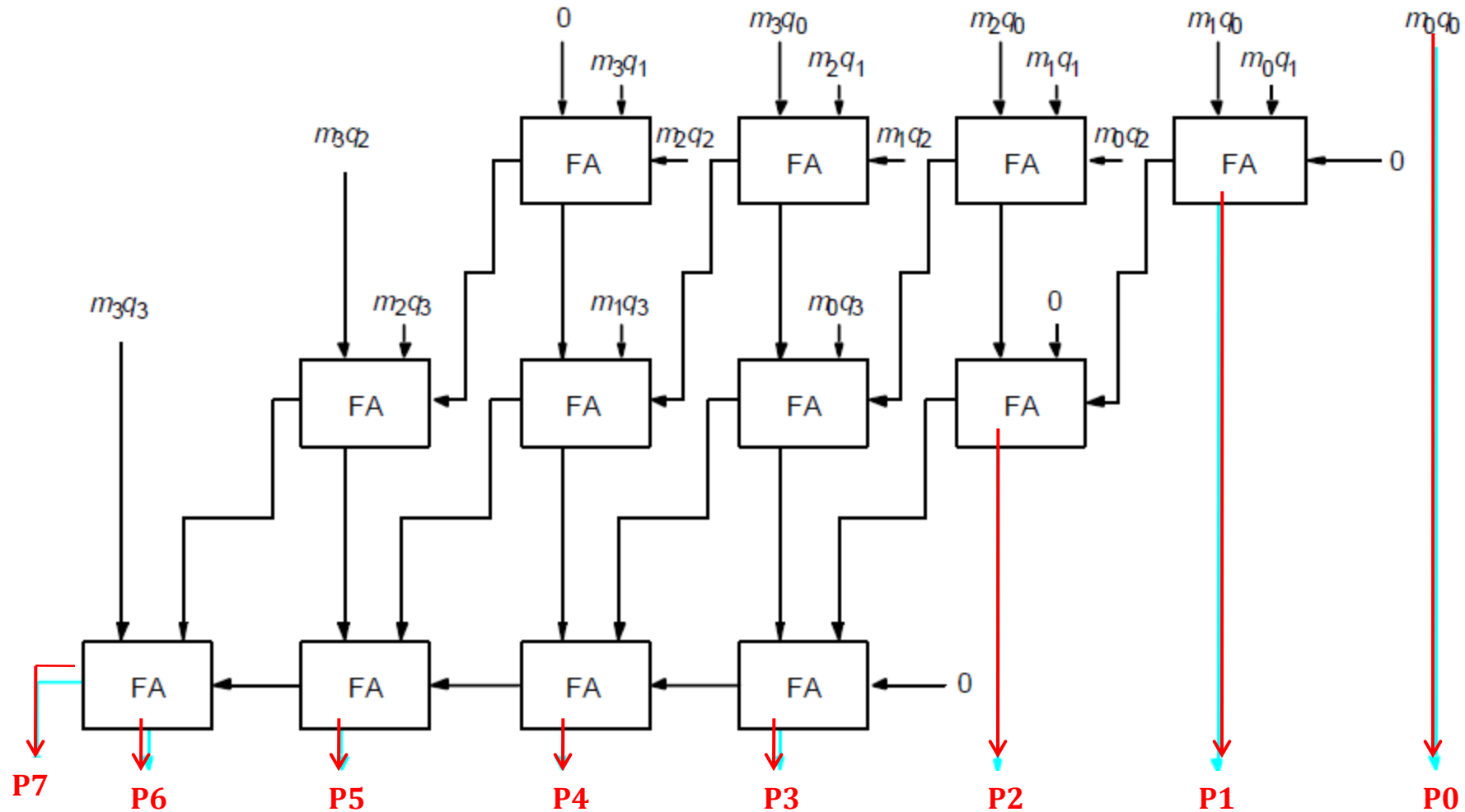

Carry-Save Addition of Summands (Cont.,)

- Consider the addition of many summands, we can:
 - Group the summands in threes and perform carry-save addition on each of these groups in parallel to generate a set of S and C vectors in one full-adder delay
 - Group all of the S and C vectors into threes, and perform carry-save addition on them, generating a further set of S and C vectors in one more full-adder delay
 - Continue with this process until there are only two vectors remaining
 - They can be added in a RCA or CLA to produce the desired product

Carry-Save Addition of Summands

						1	0	1	1	0	1	(45)	M
					x	1	1	1	1	1	1	(63)	Q
						1	0	1	1	0	1	A	
				1		0	1	1	0	1		B	
			1	0		1	1	0	1			C	
				1	0	1	1	0	1			D	
			1	0	1	1	0	1				E	
		1	0	1	1	0	1					F	
1	0	1	1	0	0	0	1	0	0	1	1	(2,835)	Product

Figure 6.17. A multiplication example used to illustrate carry-save addition as shown in Figure 6.18.

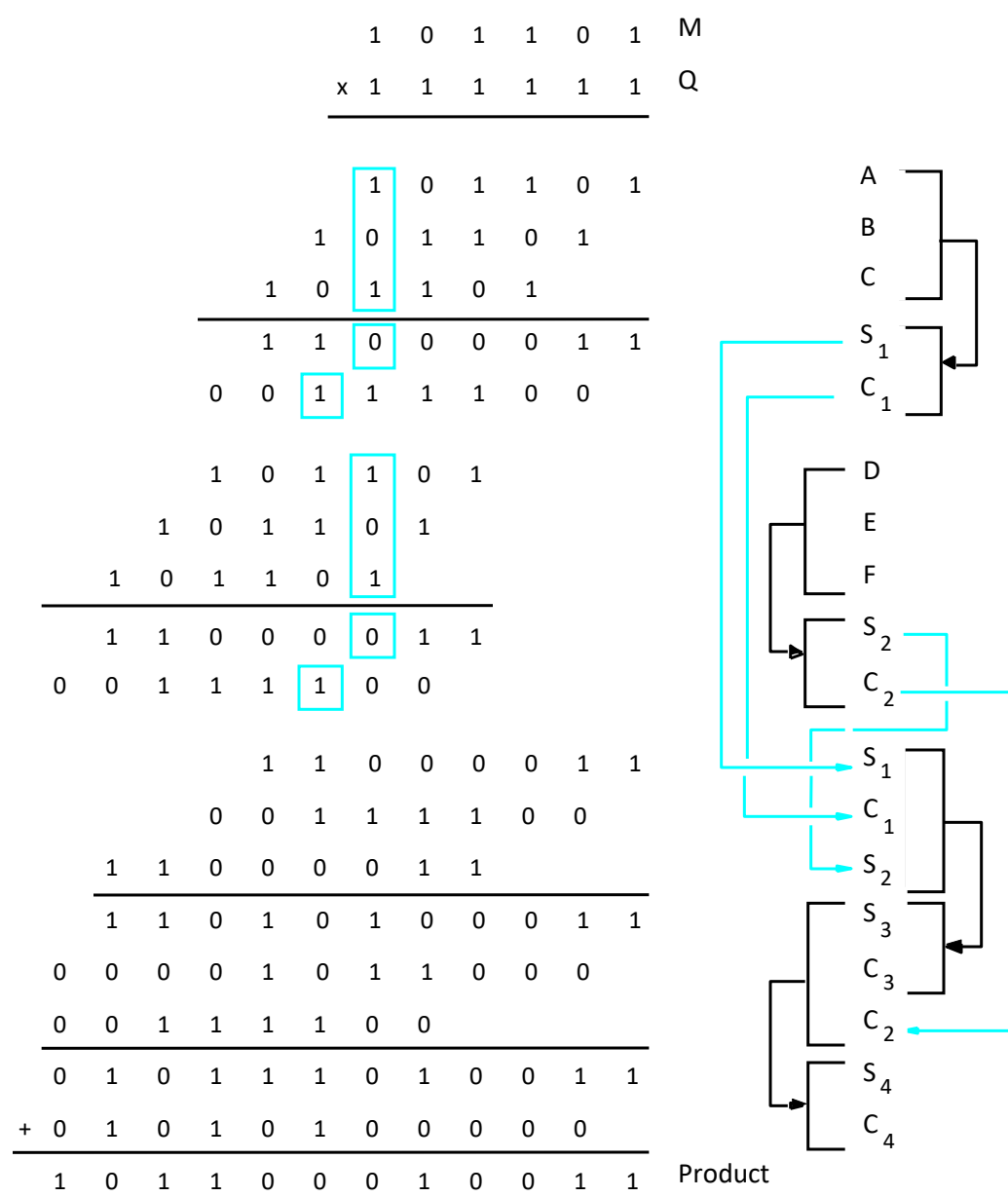


Figure 6.18. The multiplication example from Figure 6.17 performed using carry-save addition.

Integer Division

Manual Division

$$\begin{array}{r} 21 \\ 13 \overline{) 274} \\ \underline{26} \\ 14 \\ \underline{13} \\ 1 \end{array}$$

$$\begin{array}{r} 10101 \\ 1101 \overline{) 100010010} \\ \underline{1101} \\ 10000 \\ \underline{1101} \\ 1110 \\ \underline{1101} \\ 1 \end{array}$$

Longhand division examples.

Longhand Division Steps

- Position the divisor appropriately with respect to the dividend and performs a subtraction.
- If the remainder is zero or positive, a quotient bit of 1 is determined, the remainder is extended by another bit of the dividend, the divisor is repositioned, and another subtraction is performed.
- If the remainder is negative, a quotient bit of 0 is determined, the dividend is restored by adding back the divisor, and the divisor is repositioned for another subtraction.

Circuit Arrangement

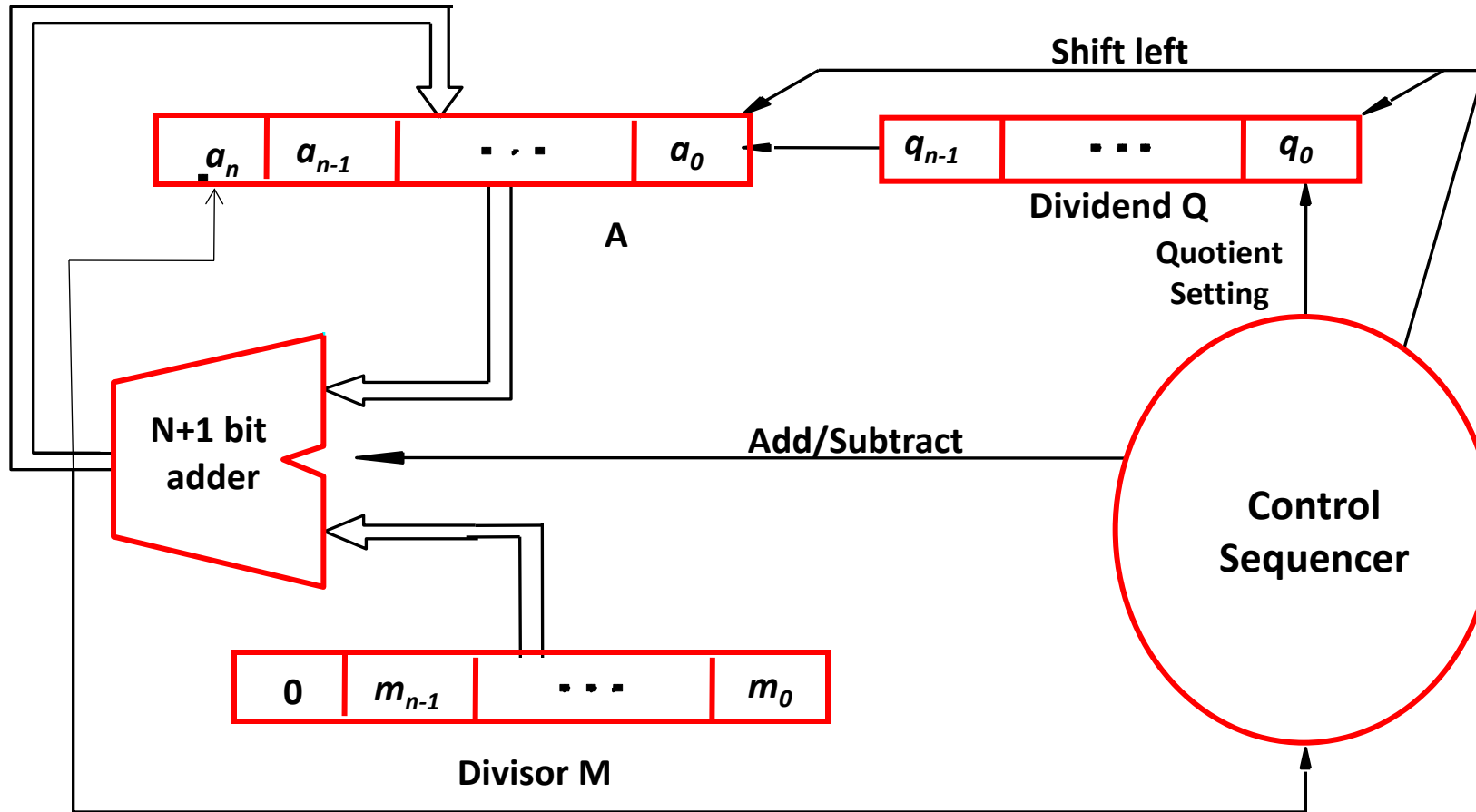


Figure 6.21. Circuit arrangement for binary division.

Restoring Division

- Shift A and Q left one binary position
- Subtract M from A, and place the answer back in A
- If the sign of A is 1, set q_0 to 0 and add M back to A (restore A); otherwise, set q_0 to 1
- Repeat these steps n times

Examples

$$\begin{array}{r}
 11 \overline{) 1000} \\
 \underline{11} \\
 10
 \end{array}$$


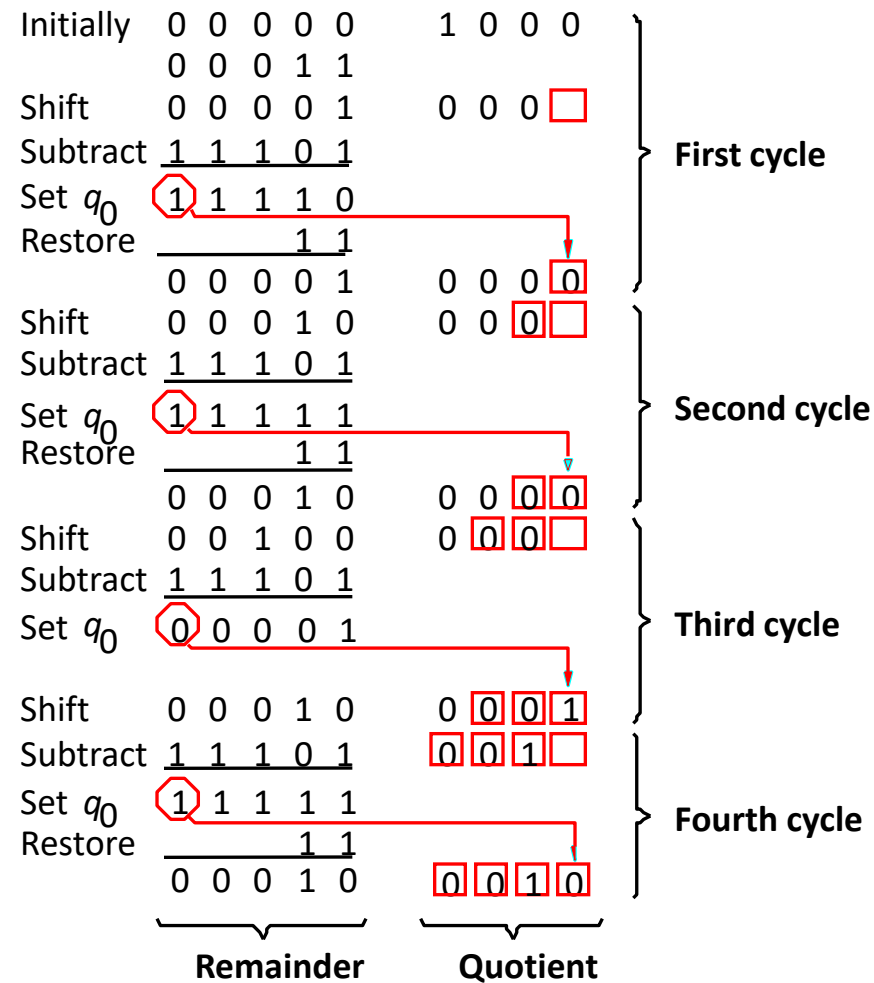


Figure 6.22. A restoring-division example.

Nonrestoring Division

- Avoid the need for restoring A after an unsuccessful subtraction.
- Step 1: (Repeat n times)
 - If the sign of A is 0, shift A and Q left one bit position and subtract M from A ; otherwise, shift A and Q left and add M to A .
 - Now, if the sign of A is 0, set q_0 to 1; otherwise, set q_0 to 0.
- Step2: If the sign of A is 1, add M to A

Examples

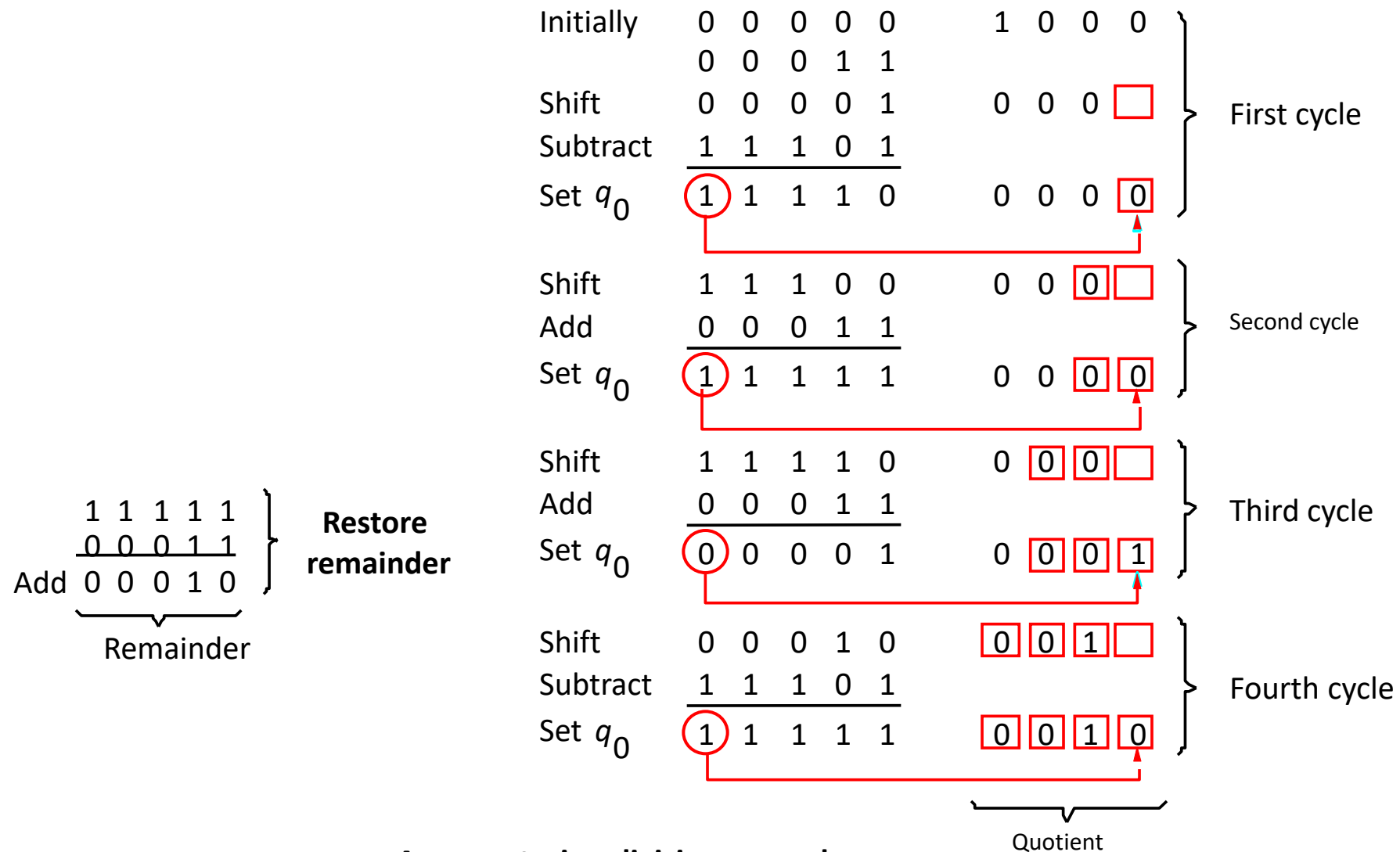

A nonrestoring-division example.